

A Single-Cycle CPU Documentation for Verilog Implementations

P4-afterclass | 2023/11/3

1. Supported Instructions

Instruction	add	sub	ori	lw	sw	beq	lui	jal	jr
Op	000000	000000	001101	100011	101011	000100	001111	000011	000000
Func	100000	100010							001000

Synchronized Reset, Overflow Not Considered

Notice:

- nop instruction must set control signals.
- Bit-width must be declared when declaring a variable of type wire.
- Remember to save the wave file when using ISim.
- Notice the brackets when connecting different width of signals, like {PC[31:28], Addr26, {2{1'b0}}}, both bit-width and brackets should be used.

2. Modules definition

(1) Program Counter

- Ports definition

Port name	Direction	Width	Description
clk	input		
reset	input		
next_PC	input	[31:0]	PC + 4/Beq/Jal/Jr ->
PC	output	[31:0]	-> Adder / GRF
InstrAddr	output	[11:0]	-> Im

▪ Behavioral Description

```

if beq && Zero then
    PC <= PC + 4 + (Sign_ext(imm16) << 2 )
else if jal then
    PC <= {PC[31:28], addr26, 00}
else if jr then
    PC <= GPR[31] # $ra
else
    PC <= PC + 4

```

(2) Instruction Memory

▪ Ports Definition

Port name	Direction	Type	Description
InstrAddr	input	[11:0]	PC ->
Instr	output	[31:0]	-> Splitter

▪ Behavioral Description

```

# 4096 * 32bit, [31:0] Reg [0:4095]
Instr = IM[InstrAddr]

```

(3) *Splitter*

■ Ports Definition

Port name	Direction	Type	Description
Instr	input	[31:0]	PC →
Addr26	output	[25:0]	Instr[25:0]
Imm16	output	[15:0]	Instr[15:0]
func	output	[5:0]	Instr[5:0]
Rd	output	[4:0]	Instr[15:11]
Rt	output	[4:0]	Instr[20:16]
Rs	output	[4:0]	Instr[25:21]
Op	output	[5:0]	Instr[31:26]

■ Behavioral Description

None.

(4) *GRF*

■ Ports Definition

Port name	Direction	Type	Description
clk	input		
reset	input		
RegWrite	input		<i>Signal</i>
pC	input	[31:0]	PC ->
WD	input	[31:0]	Ext / ALU / PC / DM ->
A1	input	[4:0]	Rs ->
A2	input	[4:0]	Rt ->
WA	input	[4:0]	Rt / Rd / 31 ->
RD1	output	[31:0]	-> ALU / PC
RD2	output	[31:0]	-> ALU / DM

■ Behavioral Description

```

RD1 <= GRF[A1]
RD2 <= GRF[A2]

if RegWrite == 1 then
    GRF[WA] <= WD

```

(5) ALU

■ Ports Definition

Port name	Direction	Type	Description
srcA	input	[31:0]	GRF ->
srcB	input	[31:0]	Ext / GRF ->
ALUop	input	[2:0]	<i>signal</i>
Zero	output		-> MUX(beq)
Result	output	[31:0]	-> GRF / DM

▪ Behavioral Description

```
if ALUop == 3'b000
    Result <= A + B
else if ALUop == 3'b001
    Result <= A - B
else if ALUop == 3'b010
    Result <= A & B
else if ALUop == 3'b011
    Result <= A | B

if A - B == 0 then
    Zero <= 1'b1
else
    Zero <= 1'b0
```

(6) Data Memory

▪ Ports Definition

Port name	Direction	Type	Description
clk	input		
reset	input		
WriteData	input		signal
ReadData	input		signal
Addr	input	[31:0]	ALU ->
WD	input	[31:0]	GRF ->
pC	input	[31:0]	PC ->
RD	output	[31:0]	-> GRF

▪ Behavioral Description

```
if WriteData == 1'b1
    RD <= DM[Addr[13:2]]
else if ReadData == 1'b1
    DM[Addr[13:2]] <= WD
```


(7) CtrlUnit

■ Ports Definition

Port name	Direction	Type	Description
op	input	[5:0]	
func	input	[5:0]	
ReadData	output		DM
WriteData	output		DM
MemToReg	output		GRF
PCsrc	output		PC
RegDst	output		GRF
ALUsrc	output		ALU
ShfToReg	output		GRF
RegWrite	output		GRF
ALUop	output	[2:0]	ALU
ExtRes	output		Extender
Jump	output	[2:0]	PC / GRF

■ Corresponding Instructions

	RegDst	ALUsrc	ALUop[1:0]	ReadData	WriteData	MemToReg	ShfToReg	RegWrite	ExtRes	Jump[1:0]
ADD	1	0	000(Add)	x	x	1	0	1	x	000
SUB	1	0	001(Sub)	x	x	1	0	1	x	000
ORI	0	1	011(Or)	x	x	1	0	1	1	000
LW	0	1	000(Add)	1	x	0	0	1	0	000
SW	x	1	000(Add)	x	1	x	0	0	0	000
BEQ	x	0	001(Sub)	x	x	x	x	0	0	000
LUI	0	x	xxx	x	x	x	1	1	x	000
JAL	0	0	xxx	x	x	0	0	1	x	010
JR	x	x	xxx	x	x	x	x	0	x	001

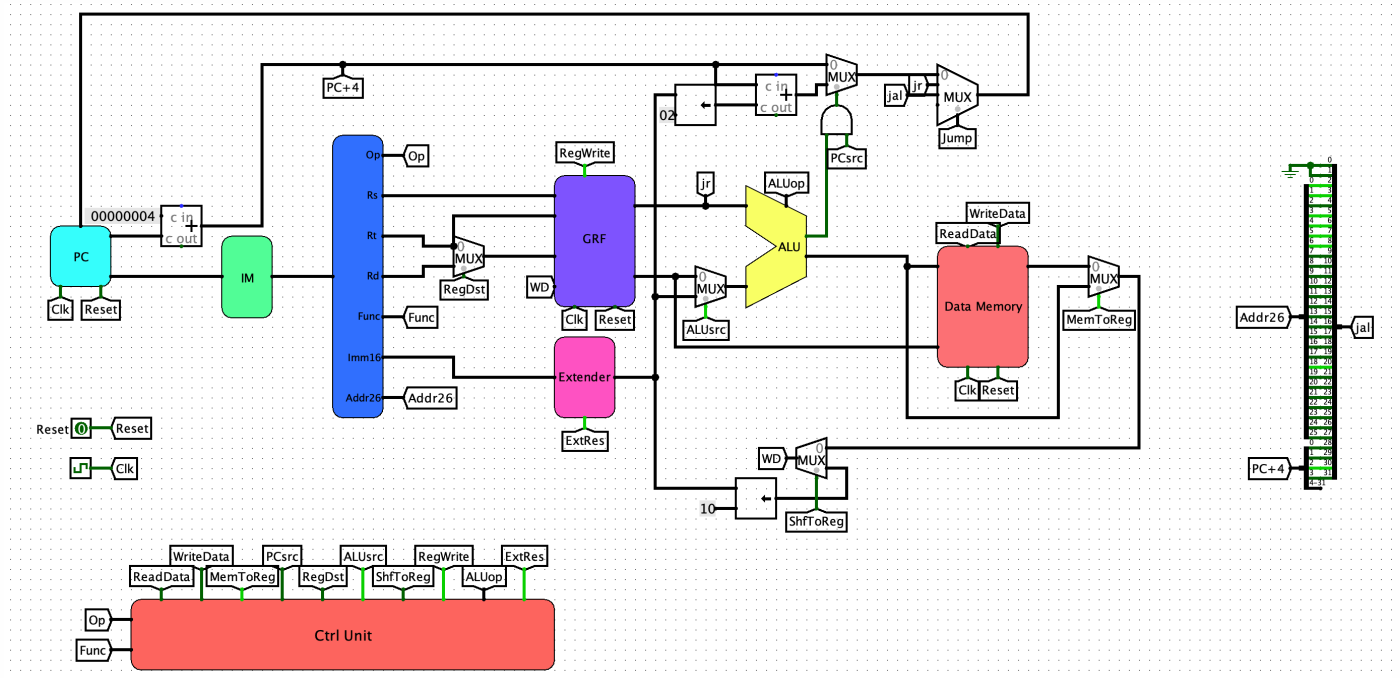

(1) DM按字寻址，而不是按字节寻址。因此数据合理的情况下，保证Addr的后两位始终为0，即Addr始终是4的倍数。该信号来自ALU。

(2) 控制信号每种取值所对应的指令:

```

wire ALUSrc;
assign ALUSrc = (instr == `ORI) || (instr == `LW) || (instr == `SW);

wire MemToReg;
assign MemToReg = (instr == `ADD) || (instr == `SUB) || (instr == `ORI);

```

优点：新增指令时较为方便；

缺点：不好全面掌握一种指令对应的信号，比较分散。

指令对应控制信号：

```
if (op == 6'b000000) begin // R
    if (func == 6'b100000) begin // add
        RegDst = 1'b1;
        ALUsrc = 1'b0;
        ALUop = 2'b00;
        PCsrc = 1'b0;
        ReadData = 1'b0; // x
        WriteData = 1'b0; // x
    end
end
```

```

        MemToReg = 1'b1;
        ShfToReg = 1'b0;
        RegWrite = 1'b1;
        ExtRes = 1'b0; // x
        Jump = 2'b00;
    end
    else if (func == 6'b100010) begin // sub
        RegDst = 1'b1;
        ALUsrc = 1'b0;
        ALUop = 2'b01;
        PCsrc = 1'b0;
        ReadData = 1'b0; // x
        WriteData = 1'b0; // x
        MemToReg = 1'b1;
        ShfToReg = 1'b0;
        RegWrite = 1'b1;
        ExtRes = 1'b0; // x
        Jump = 2'b0;
    end
end

```

优点：每种指令对应的控制信号比较清晰，方便调试。

缺点：代码冗杂，新增控制信号或者新增指令时比较繁琐，可扩展性稍差。

(3) 同步复位时：

```

always @(posedge clk) begin
    if (reset == 1'b1) begin
        // do something
    end
    else begin
        // do something
    end
end

```

异步复位时：（假定复位信号高电平有效）

```

always @(posedge clk or posedge reset) begin
    if (reset == 1'b1) begin
        // do something
    end
    else begin
        // do something
    end
end

```

敏感信号列表不同，在同步复位中复位信号优先级小于时钟信号，而在异步复位中两种信号优先级一致。

(4) 在忽略了溢出的情况下，**add**指令不会检查运算结果是否溢出，那么指令等效于**addu**。同样的，如果忽略溢出，那么**addi**指令也不会检查结果是否溢出，这就与**addiu**本质上是相同的指令。

Appendice

Test_1

```
.text
    ori $t0, $zero, 0    # ori test
    ori $t0, $zero, 0xabcd
    ori $t1, $t0, 0x1234
    ori $t1, $zero, 12
    ori $t0, $zero, 0xffff

    lui $t0, 0xffff     # lui test
    lui $t1, 17
    lui $zero, 0xa

    lui $t0, 0
    ori $t0, $zero, 0x1234
    add $t0, $zero, $t0   # add test
    add $t0, $t0, $t0
    add $zero, $t0, $t0

    sub $t0, $t0, $zero   # sub test
    sub $t1, $t0, $t1
    sub $t1, $t1, $t1

    lui $t0, 0
    lui $t1, 0
    ori $t0, 12
    ori $t1, 0x1234
    sw $t1, 0($t0)        # sw test
    sw $t1, -4($t0)
    sw $t1, 4($t0)

    lui $t1, 0
    lw $t1, 0($t0)        # lw test
    lui $t1, 0
    lw $t1, 4($t0)
    lui $t1, 0
    lw $t1, -4($t0)

previous:
    lui $t0, 0
    lui $t1, 0
    ori $t0, 1
    beq $t0, $t1, jump
    beq $t1, $t1, jump

jump:
    ori $t0, $zero, 0xabcd
```

```
beq $t0, $zero, previous
beq $zero, $zero, previous
```

Test_2

```
.text
jal func2

func1:
jr $ra

func2:
jal func      # jump to func and save position to $ra
jal func1
jr $ra        # jump to $ra

func:
jr $ra        # jump to $ra
```

Test_3

```
.text
ori $t0, $zero, 0xabcd
ori $t1, $zero, 0x1234

beq $t0, $t1, func
jal func1
beq $zero, $zero, func
func:
jal func1
func1:
jr $ra
```

Test_4

```
.text
ori $t0, $zero, 1
ori $t1, $zero, 2

add $t0, $t0, $t0
add $t1, $t0, $t1

sub $t1, $t1, $t0
sub $t0, $t0, $zero

jal func
```

```
beq $zero, $zero, branch
```

```
func:
```

```
lui $t0, 0
```

```
lui $t1, 0
```

```
ori $t1, 0x1234
```

```
sw $t1, 4($t0)
```

```
lw $t0, 4($t0)
```

```
jr $ra
```

```
branch:
```

```
ori $t0, $zero, $zero
```